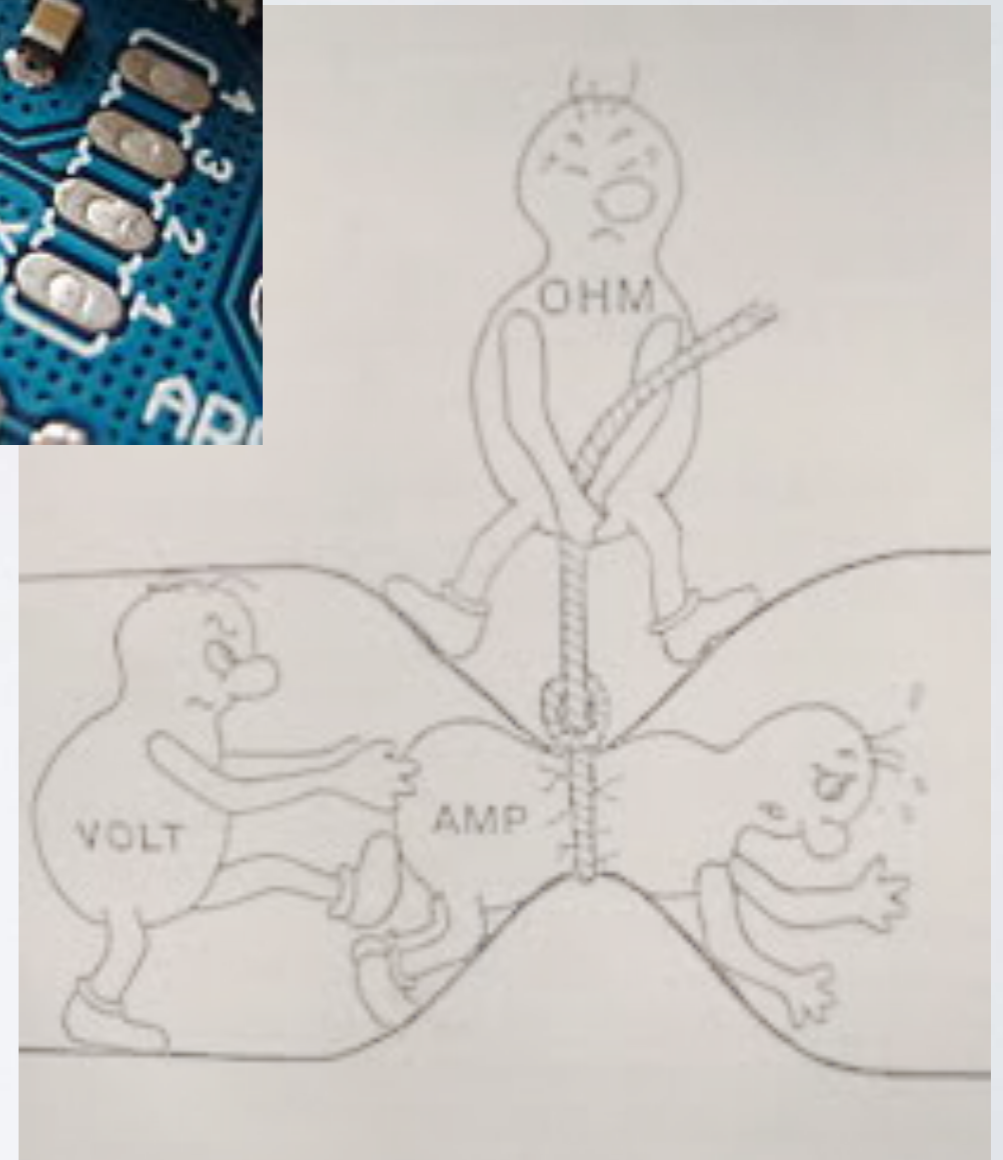



Introduction to Electronics
Artscience BA1 2020-2021
Part II



Ohm's Law:

$$U = I * R$$

(Volt)

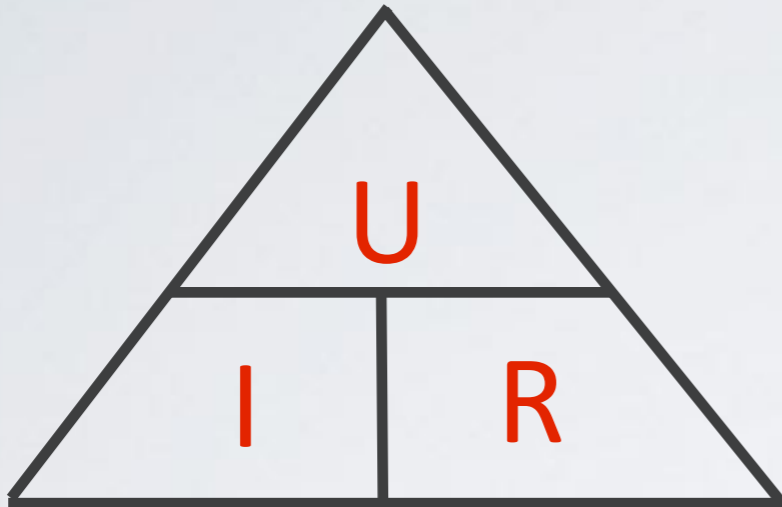


$$I = \frac{U}{R}$$

(Ampere)

$$R = \frac{U}{I}$$


(Ohm)

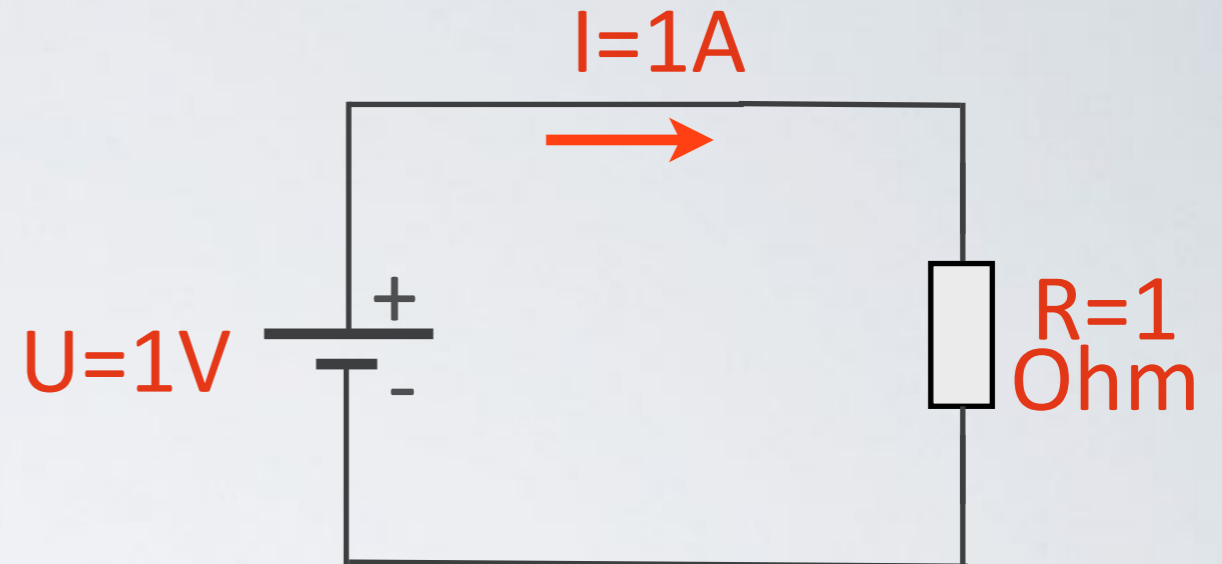

A source of 1 Volt [V] and a resistor of 1 Ohm, will result in a current of 1 Ampere [A]

2nd Kirchhoff's law:

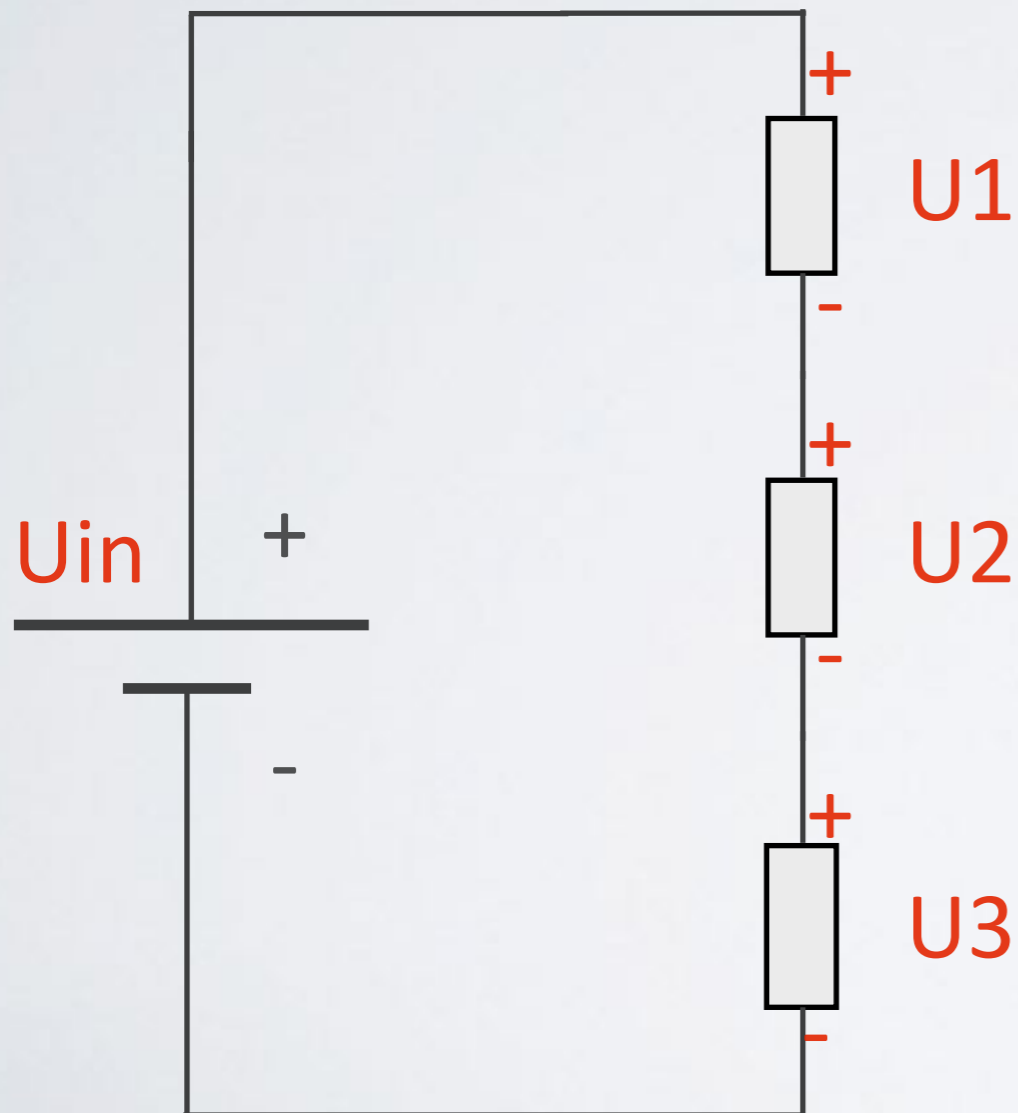The sum of all voltages inside a closed circuit are equal to 0.




$$U_{in} = U1 + U2 + U3$$

1 st Kirchoff's law:

At any node (junction) in an electrical circuit, the sum of the currents flowing into that node is equal to the sum of currents flowing out of that node.

In other words: the sum of the current in that node = 0


$$I_1 + I_2 + I_3 = I_4$$

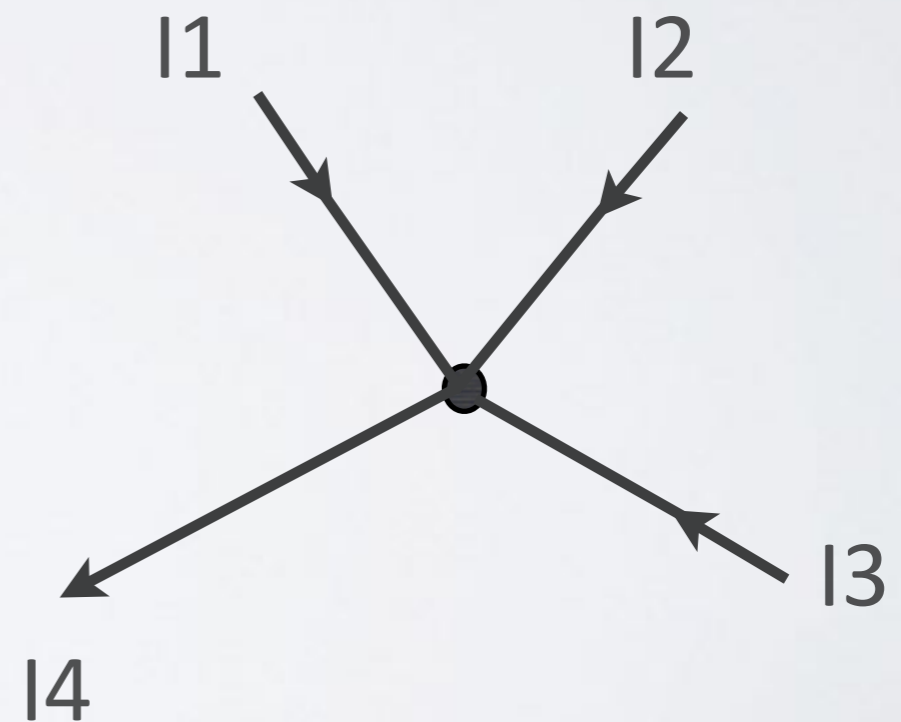

Introduction to Electronics


When resistors are placed in series, the **total resistance** will **increase** (bigger).

*The **voltage** will be divided.*

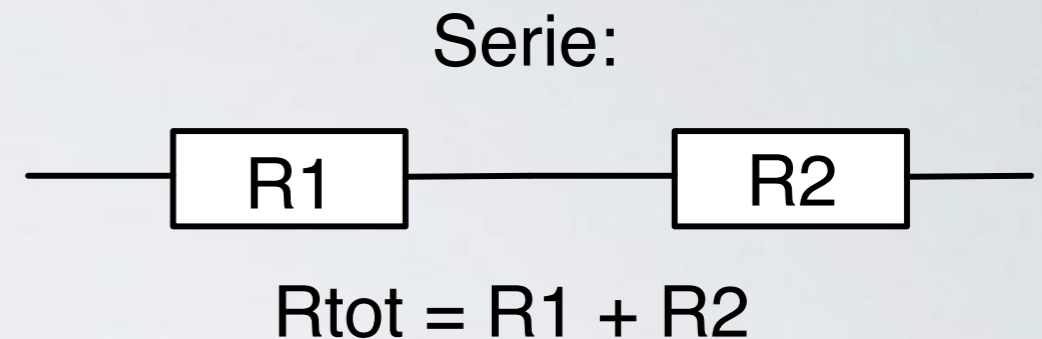


When resistors are placed in parallel, the **total resistance** will **decrease** (smaller).

*The **current** will be divided.*

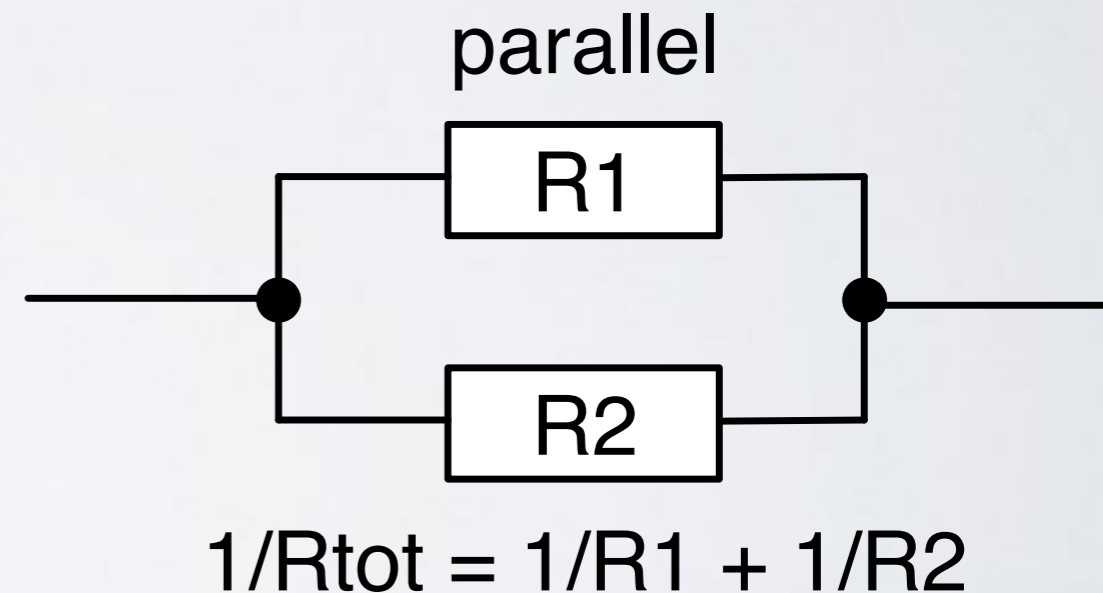



Multimeters ...

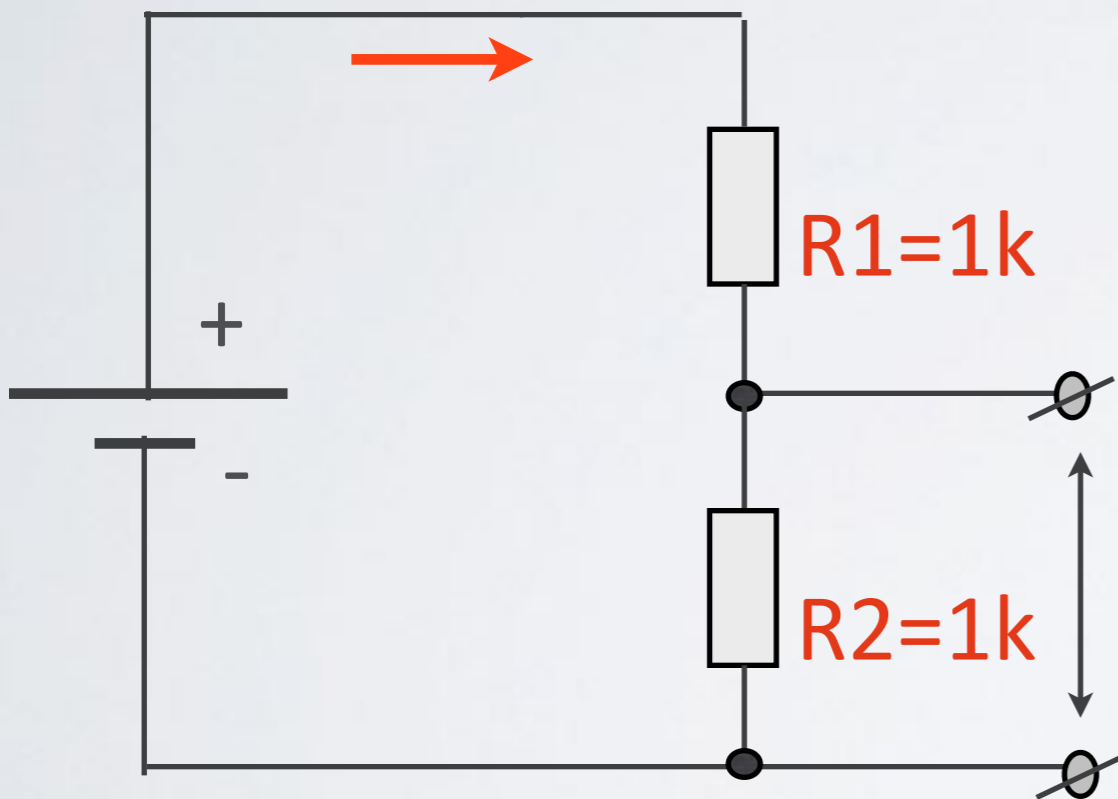

A


Current measurement
R in = 0 Ohm
Always connect in Series

V

Voltage measurement
R in = very high
Always connect parallel



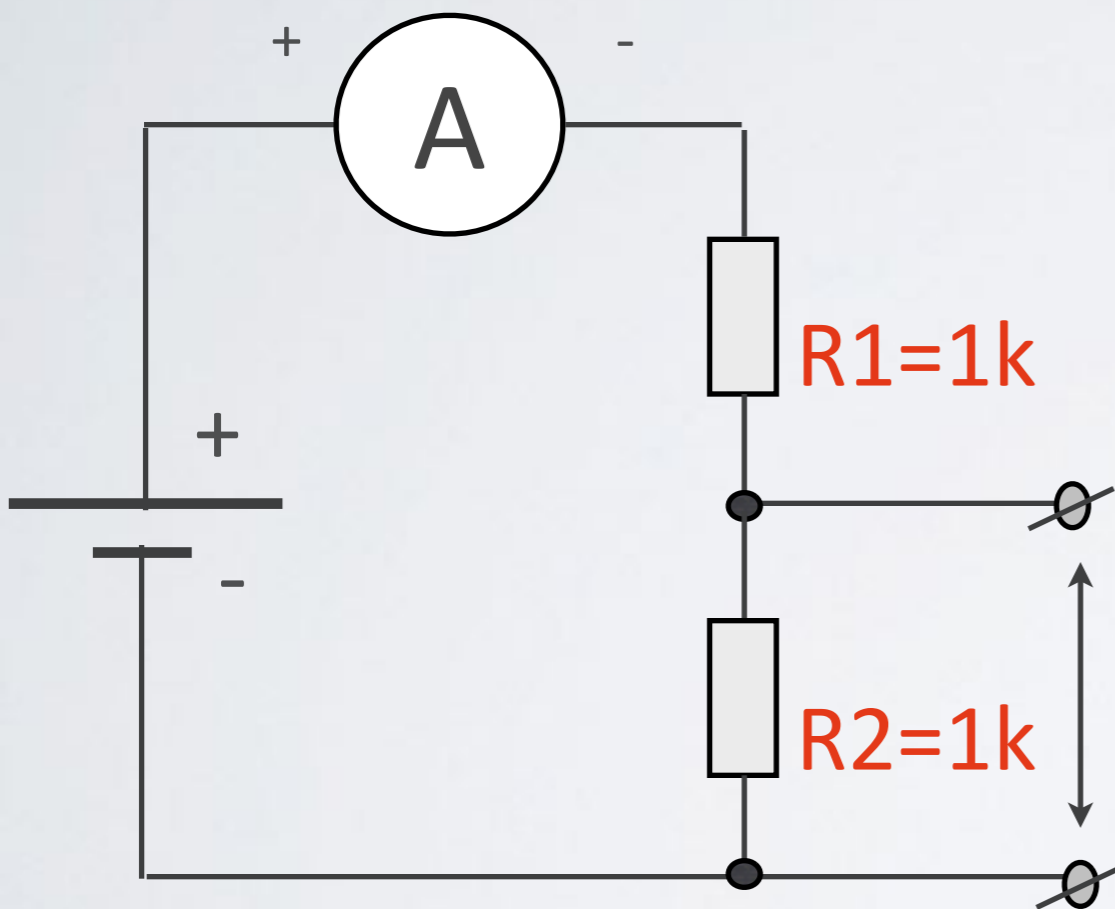
To measure the **current** with a multimeter, you have to connect the meter in **SERIES** with the wire. This means you have to disconnect the wire and place the multimeter in **BETWEEN...**



Current measurement
R in = 0 Ohm
Always connect in Series



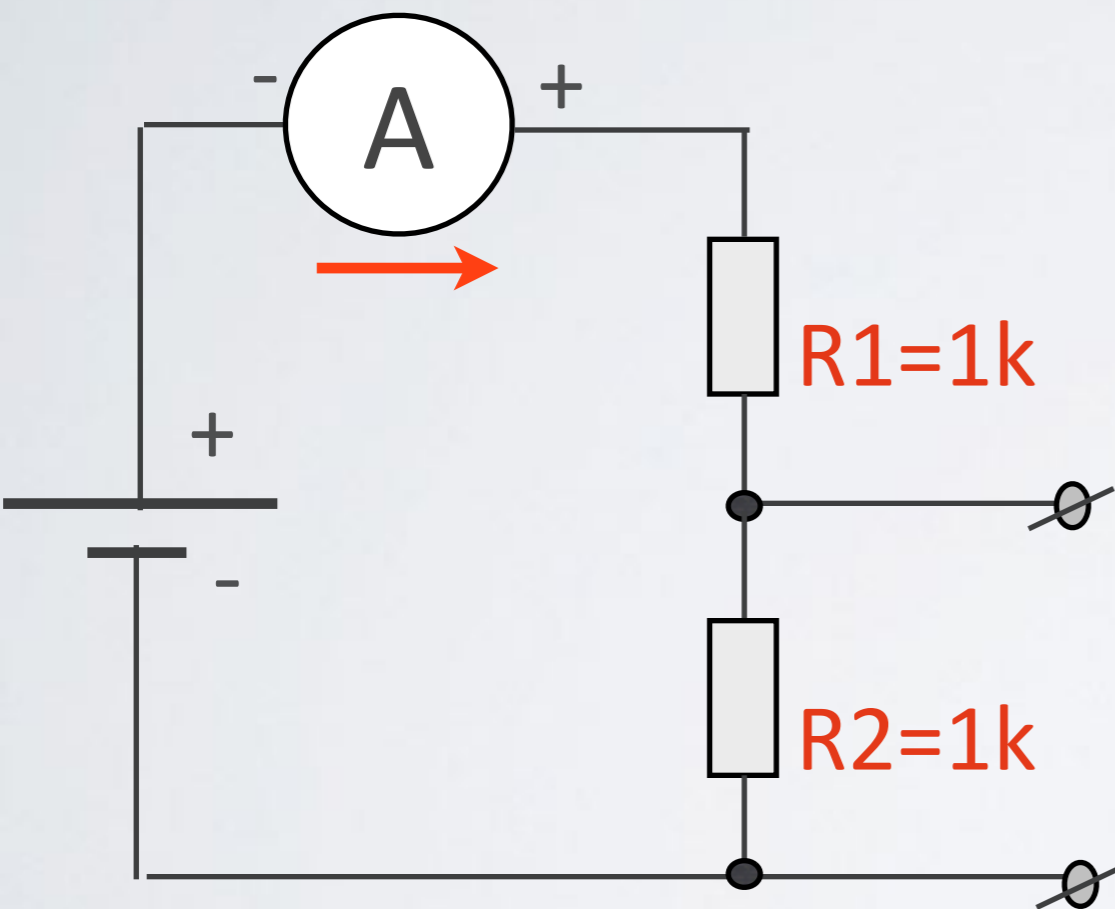
To measure the **voltage**, the multimeter has to be connected **parallel**



Voltage measurement
R in = very high
Always connect parallel



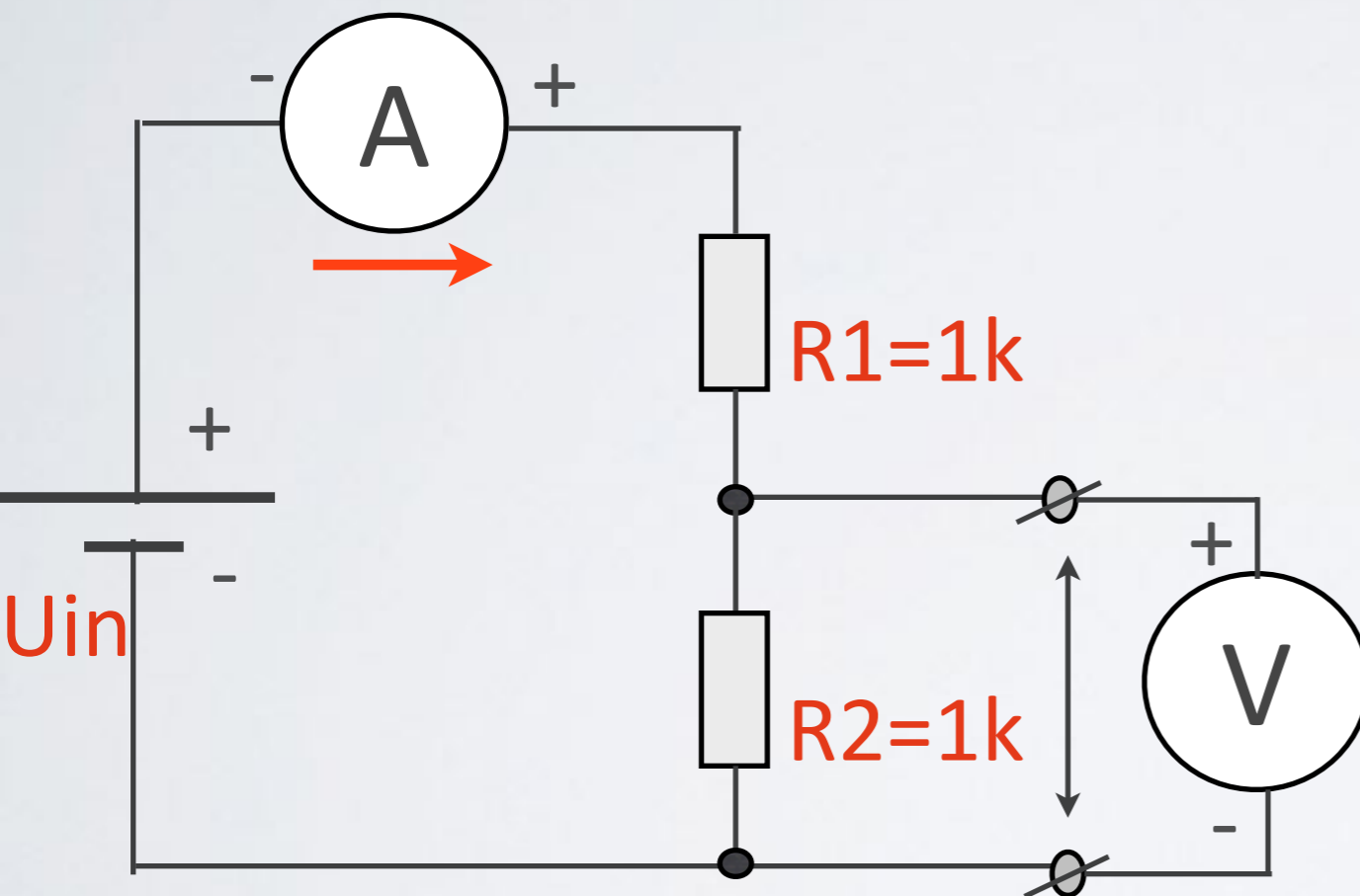To measure the **voltage**, the multimeter has to be connected **parallel**



Voltage measurement
 $R_{in} = \text{very high}$
Always connect parallel

To measure ac and dc signals, we make use of an oscilloscope




To measure ac (dc) signals, we make use of an oscilloscope

The screen is divided into divisions

The vertical axis is the amplitude

The horizontal axis is the time


Amplitude (V/div)

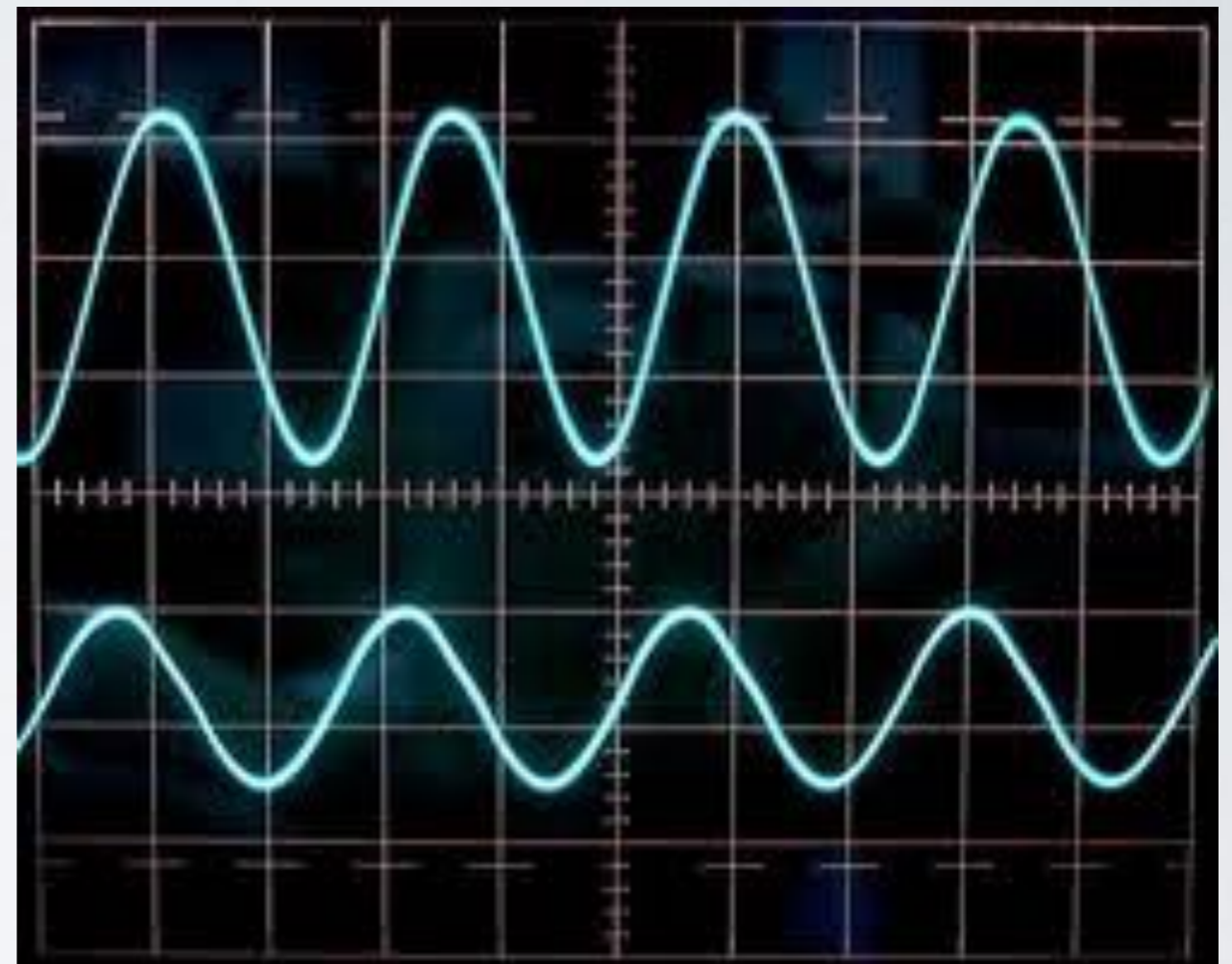

Time (m/u/Sec/div)

To measure ac & dc signals, we make use of an oscilloscope

reminder:

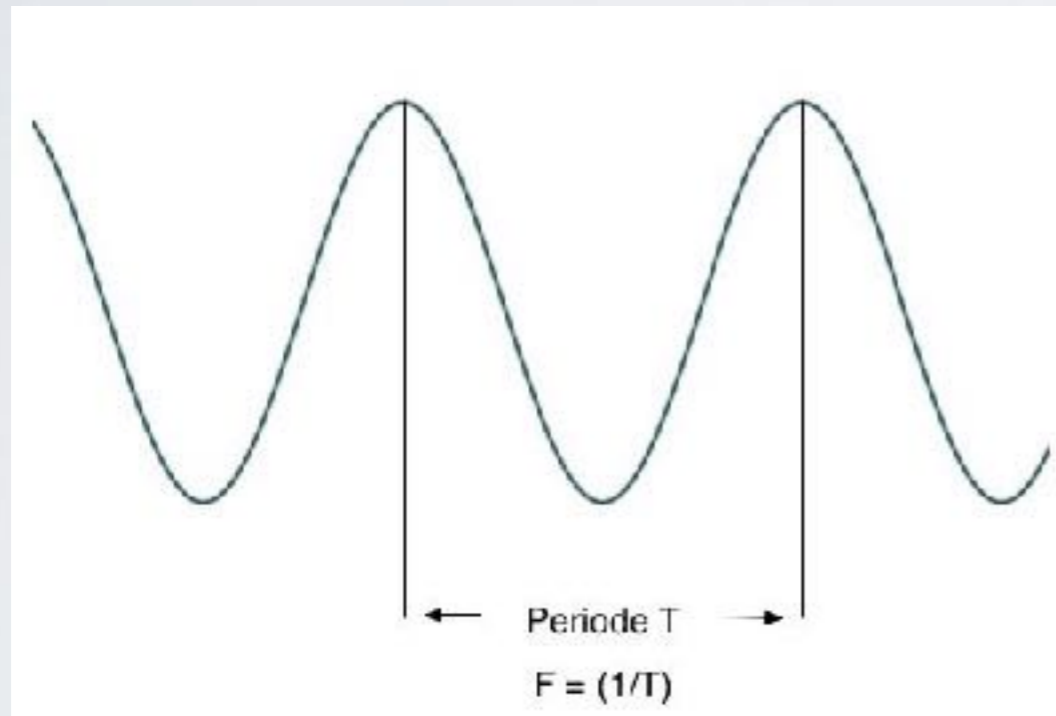

F = Frequency [Hz]

T = Cycle [Sec]

$F = (1/T)$ en $T = (1/F)$


Power Supply



Power Supply


DC ... Direct Current.

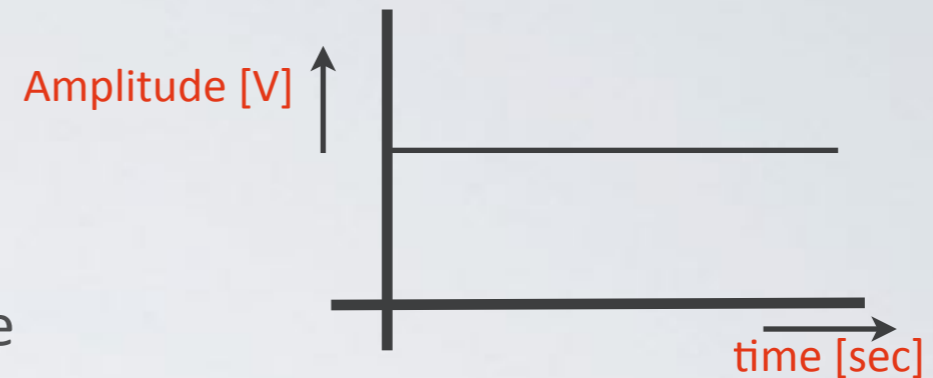Over time the value does not change its value
It's constant.




AC ... Alternating Current.

Over time the signal changes polarity

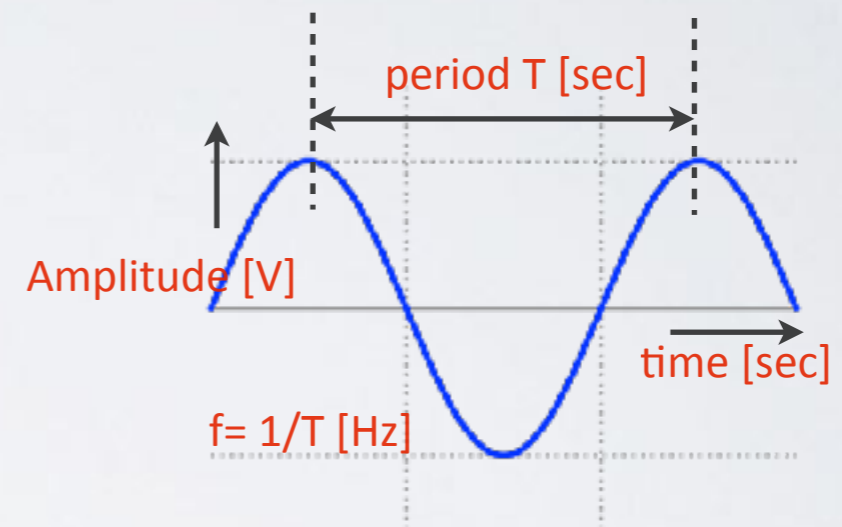



The mains connection in Europe is 230V ~ / 50Hz

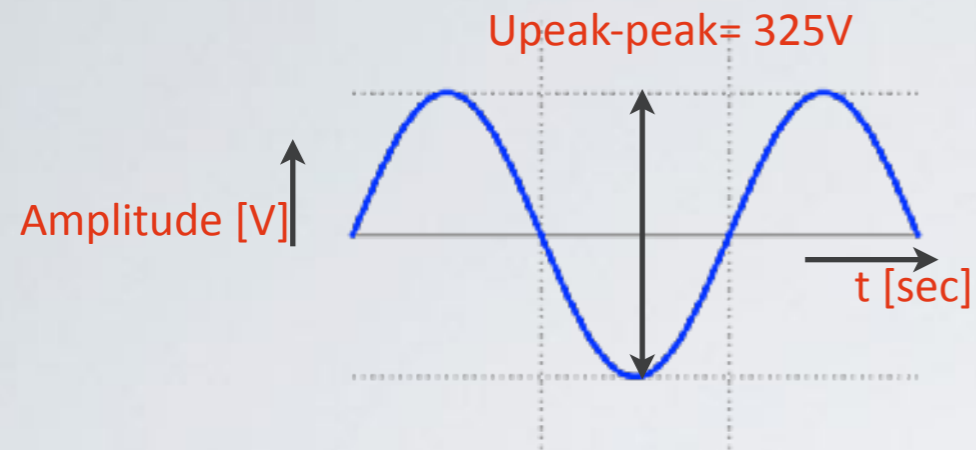The mains connection in the USA is 110V ~ / 60Hz



The mains connection on the wall provides us with 230V~ AC /50Hz.

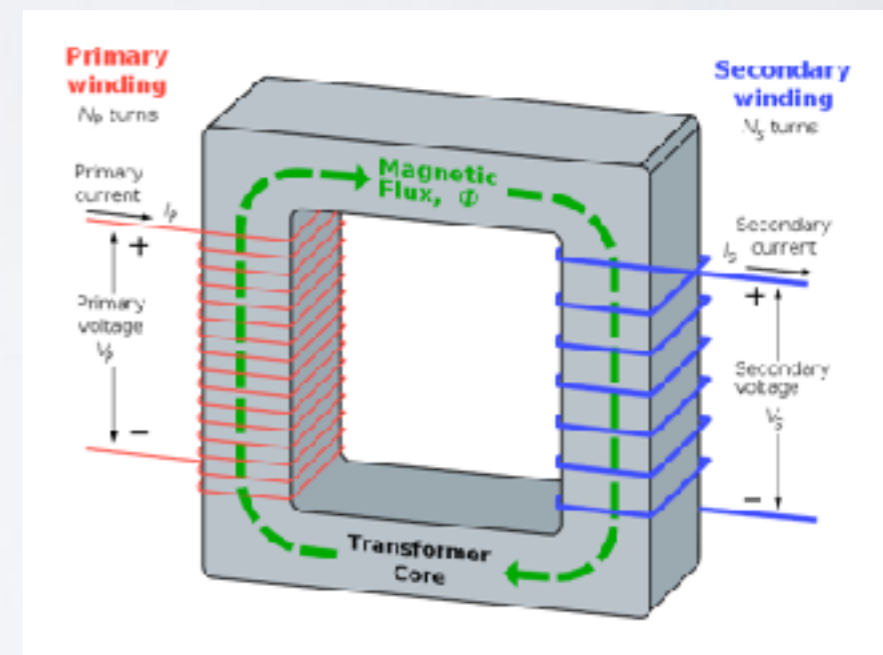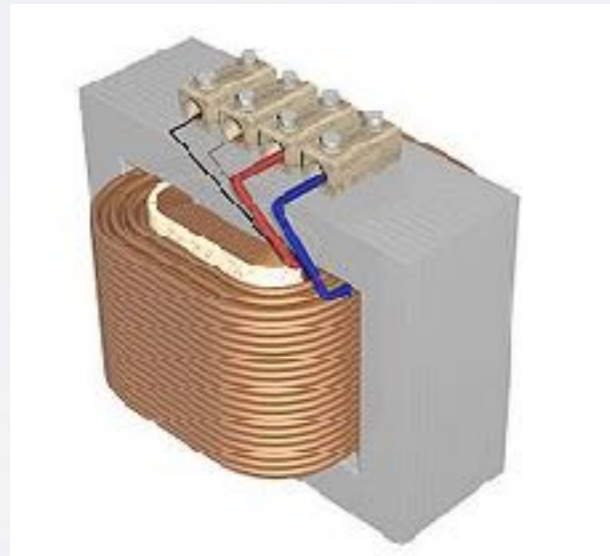If we want to create low voltage DC (e.a.12V), we have to **TRANSFORM** the voltage down with a **TRANSFORMER**:



Primary winding

N_P turns

Primary current

I_P

Primary voltage
 V_P

+

-

Secondary winding


N_S turns

Secondary current
 I_S

Secondary voltage
 V_S



+

-

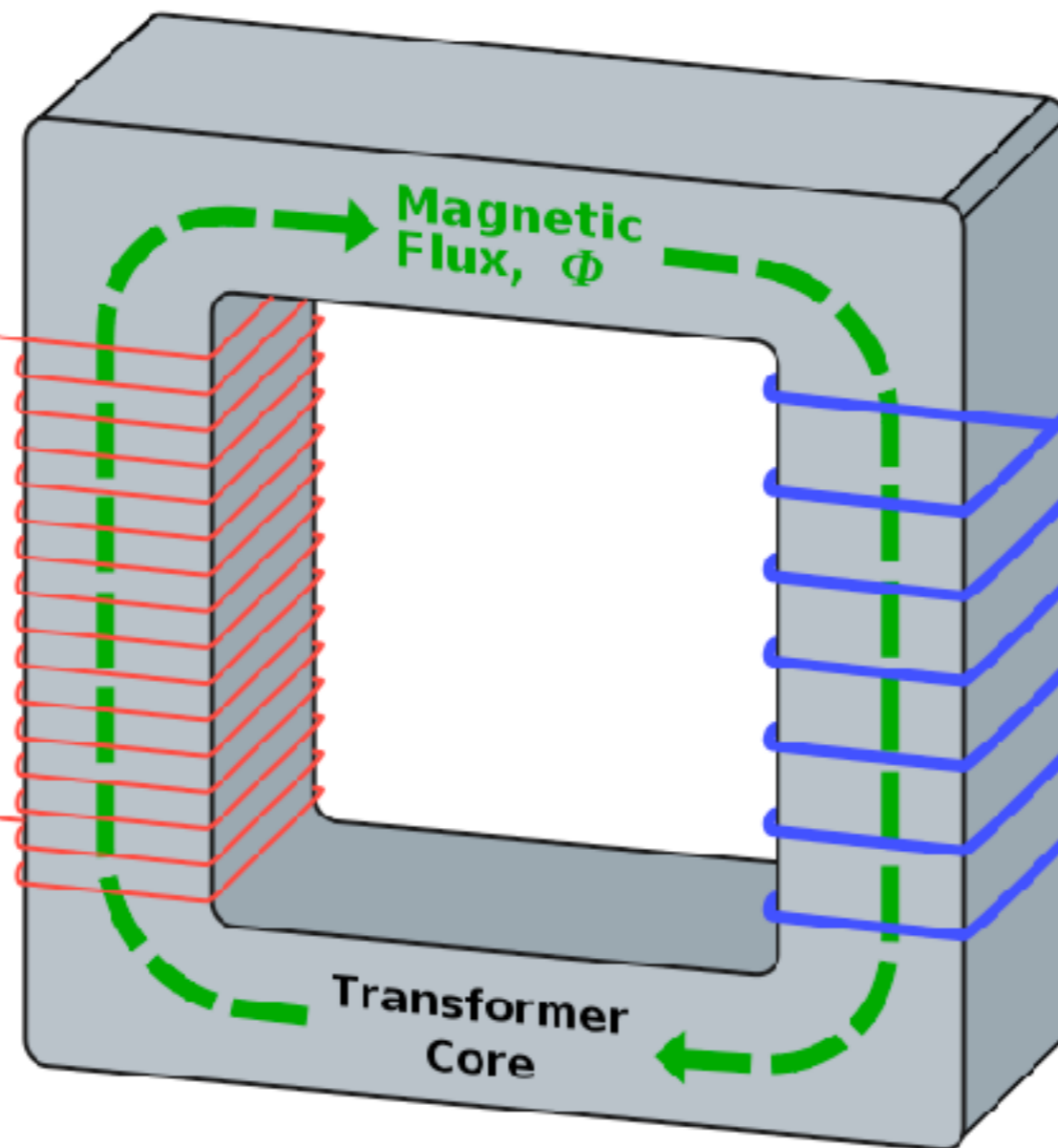

primary side

220V~/50Hz

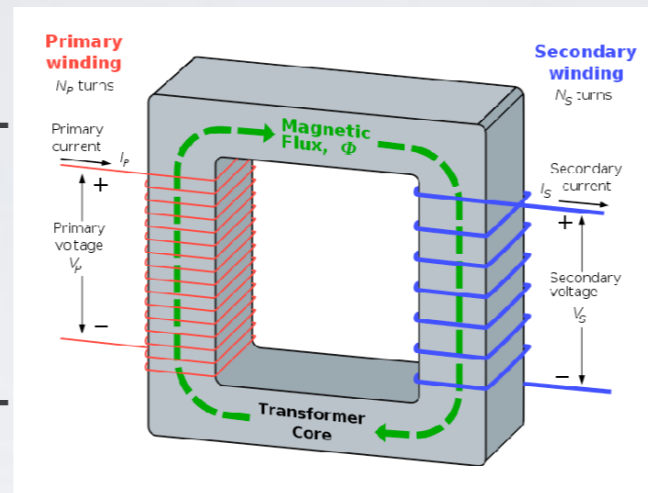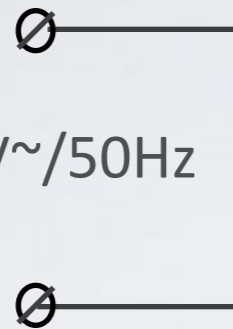


secondary side


12V~/50Hz




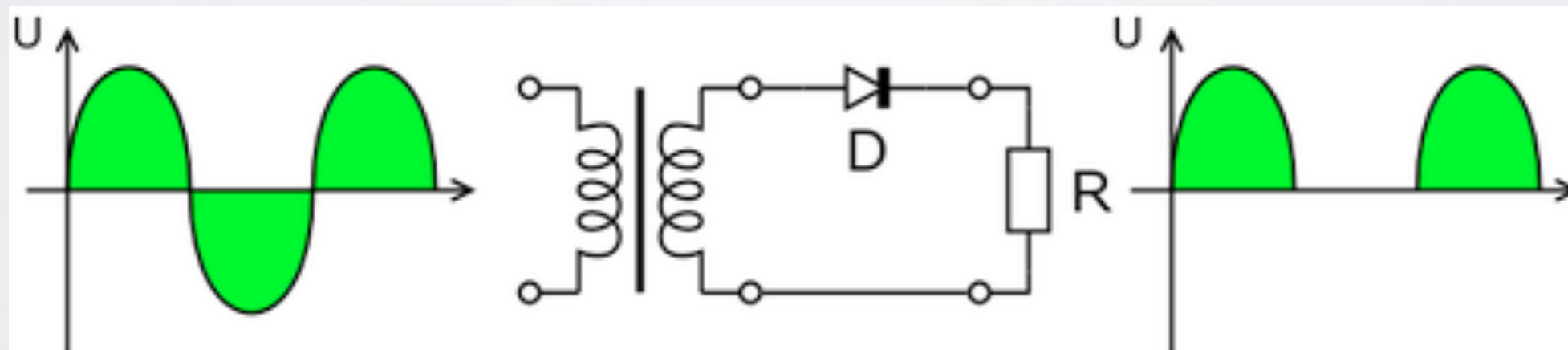
The lower value still is an AC signal. We need to **RECTIFY** this signal, in order to create a DC signal. We realize this with a rectifier circuit.



Full wave rectification

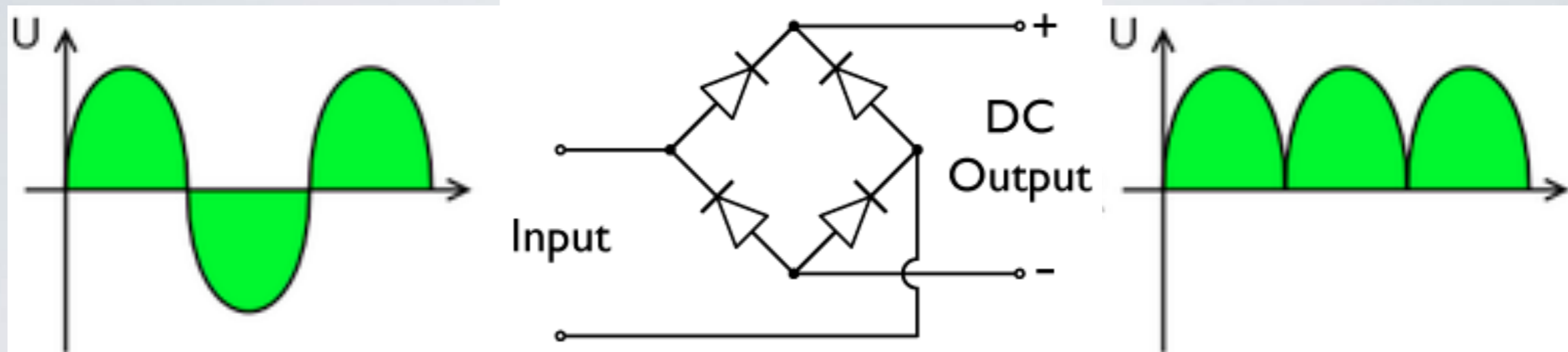

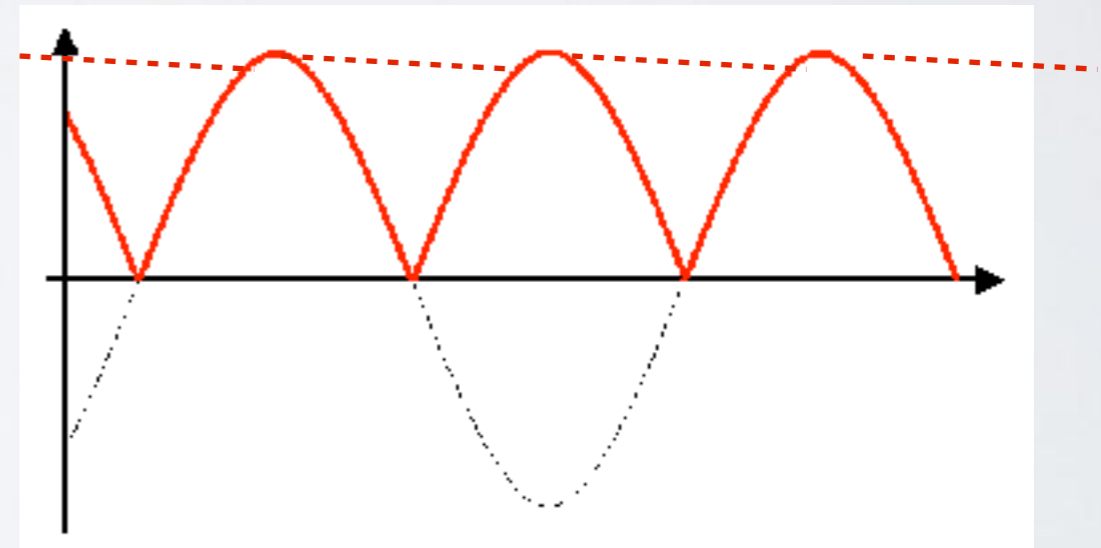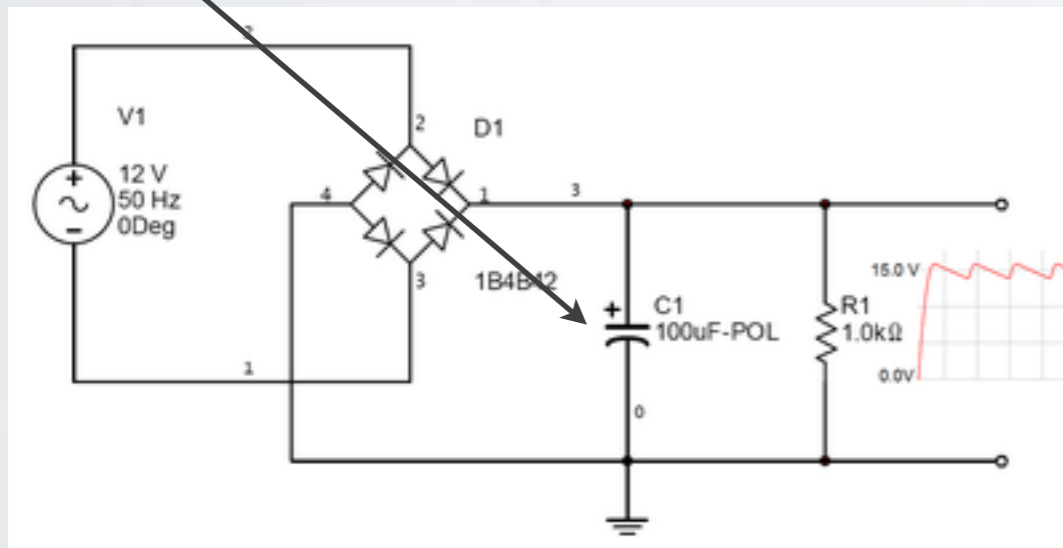A **capacitor** is used to smooth the signal




What is a capacitor?



A **capacitor** or **condenser** is a passive electronic component consisting of a pair of conductors separated by a dielectric.

Capacitors are widely used in electronic circuits to block the flow of direct current (DC) while allowing alternating current (AC) to pass or to filter out interference, **to smooth the output of power supplies** and for many other purposes.


symbol

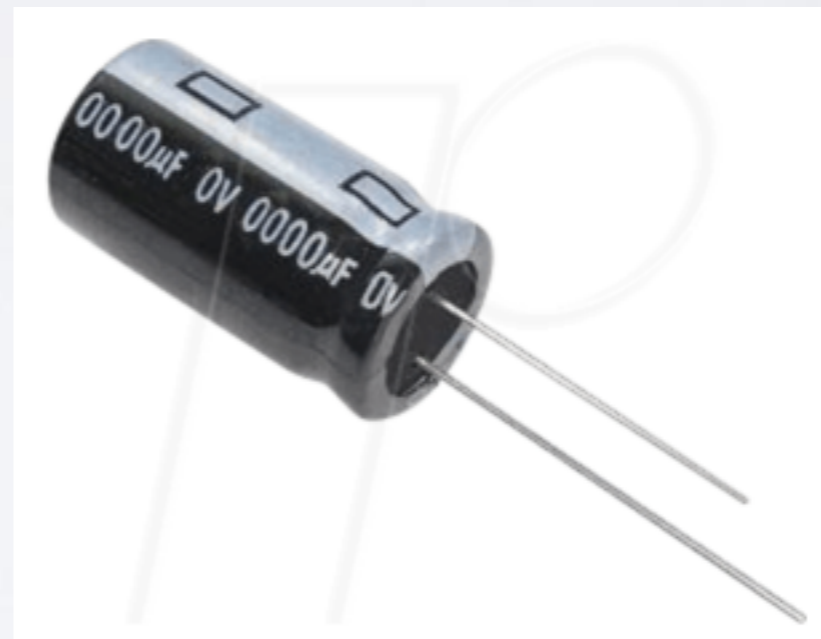


Capacitors

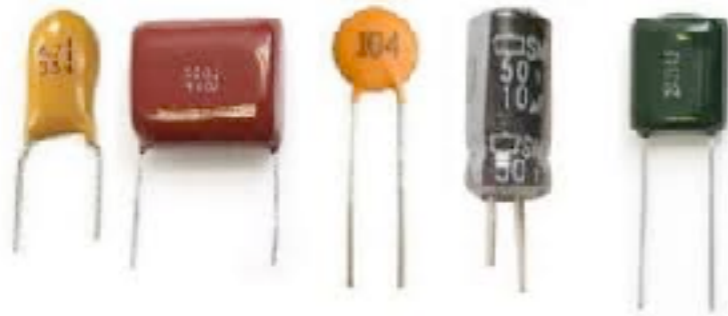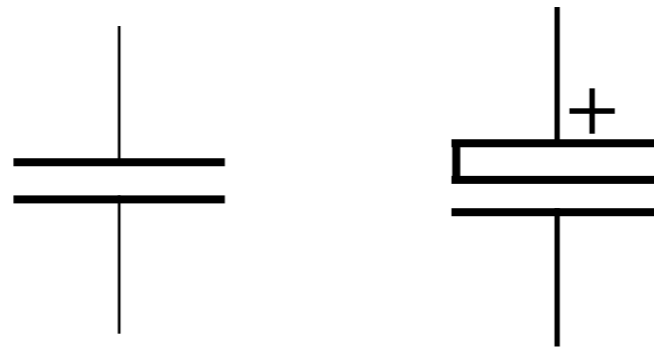

Not
connected

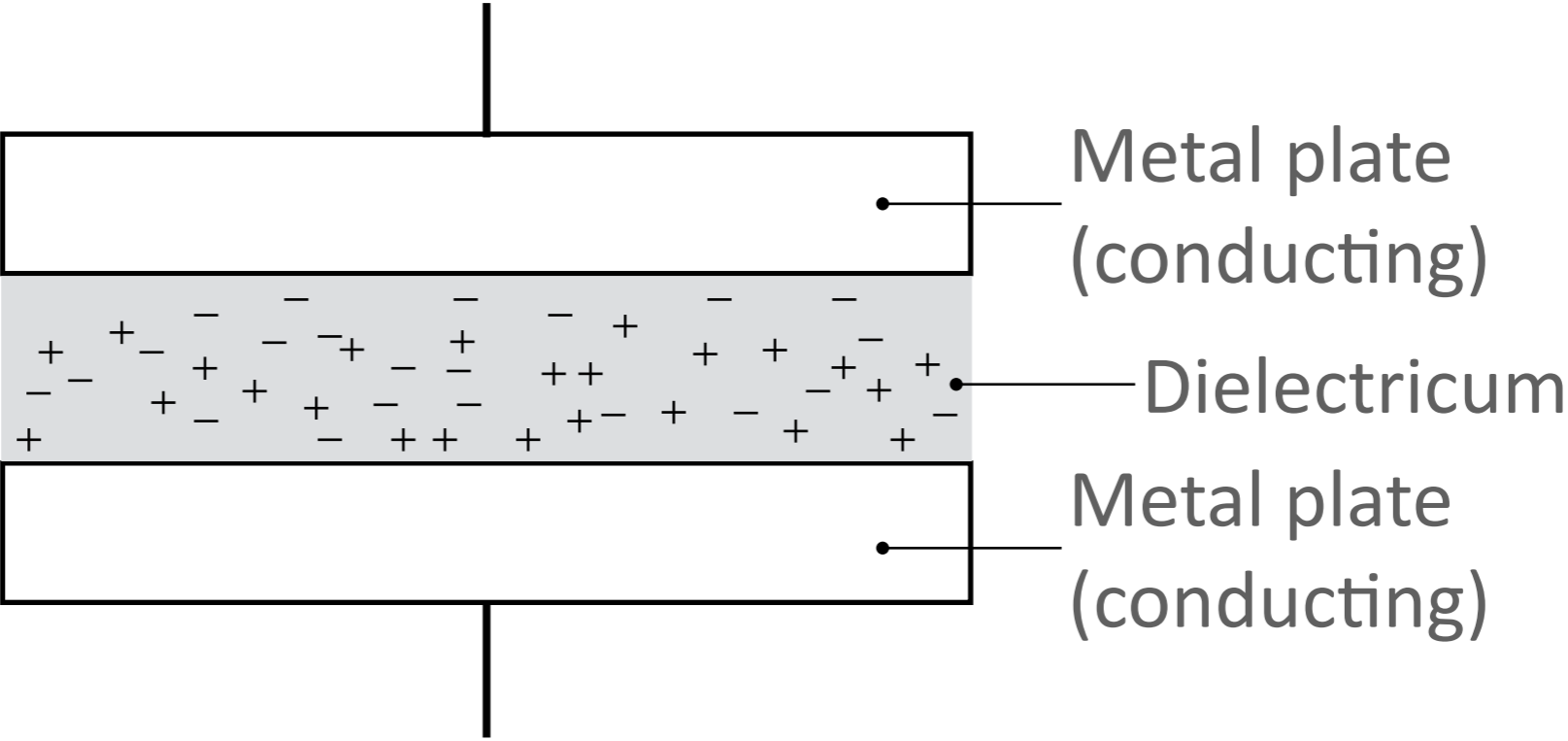

Connected to a **DC-**
source

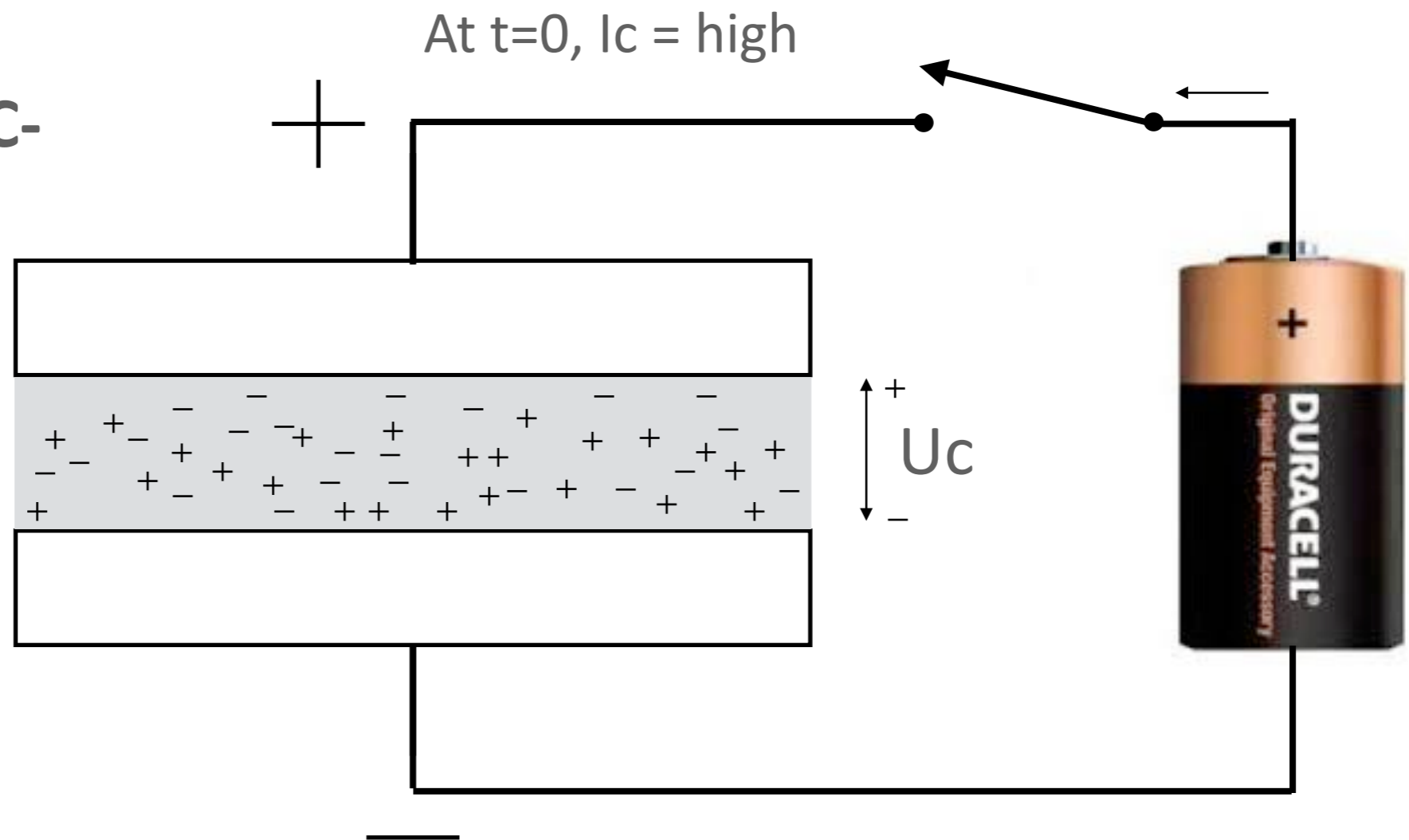


The capacitor will charge until $U_c = U_{\text{battery}}$

The charge current is very high (at time=0 sec)

For AC voltage, the Capacitor is a conductor or a resistor

Connected
to a battery

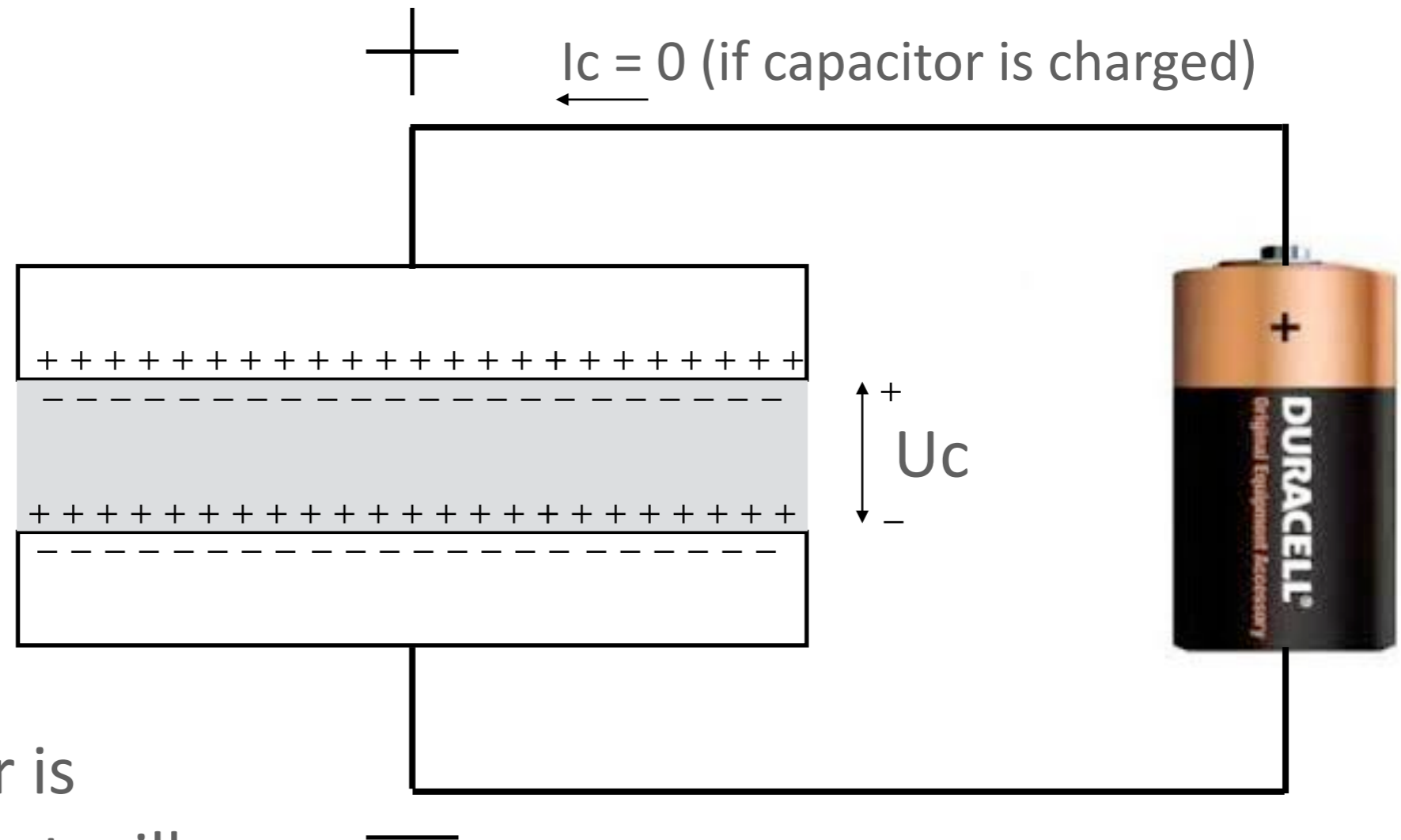The capacitor
will charge until
 $U_c = U_{\text{battery}}$




After the capacitor is
charged, the current will
be zero.

**For DC voltage, the Capacitor is a blockade (very high resistor) -
the current is zero**

Connected to an **AC**
source


The capacitor
will charge
and discharge

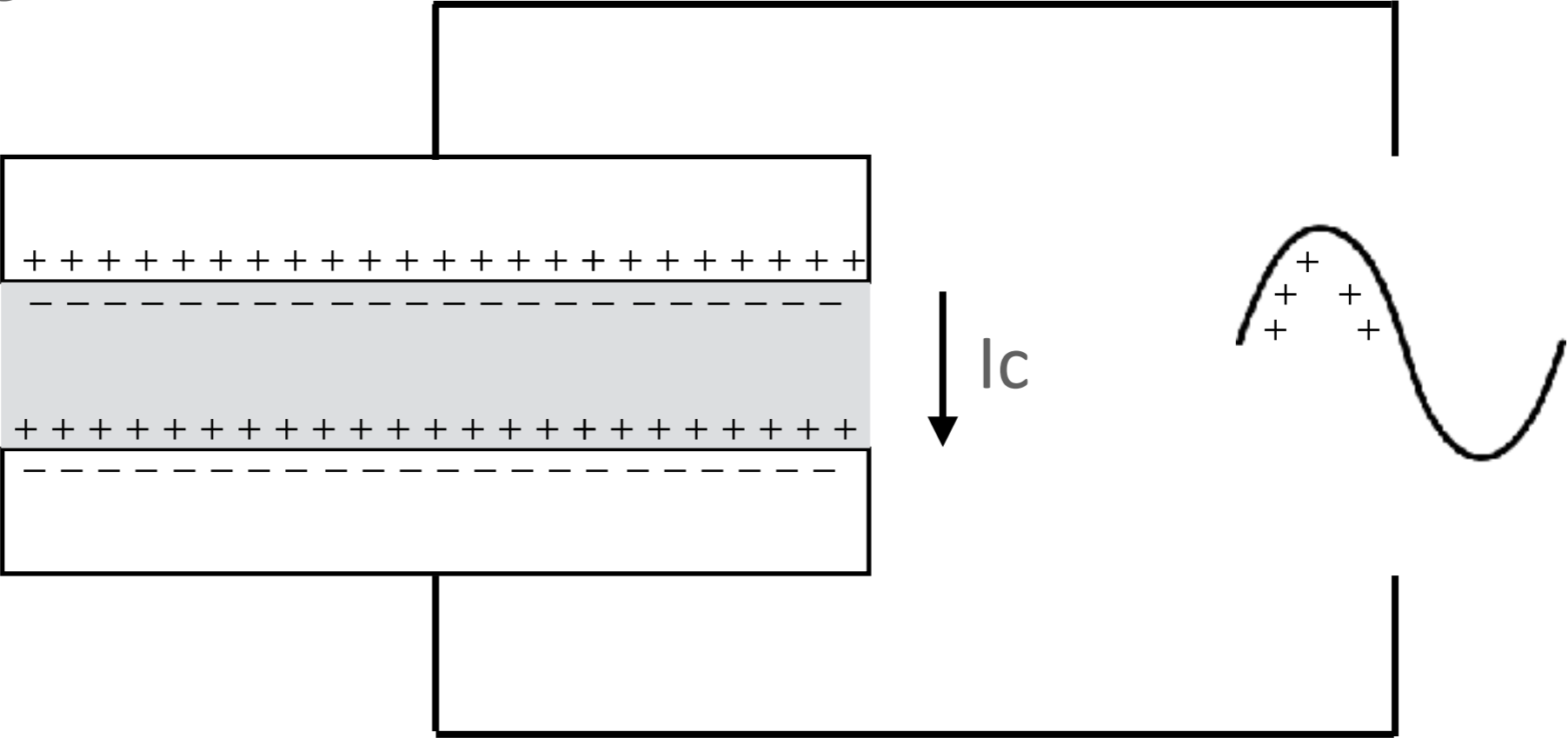

For AC voltage, the Capacitor is a conductor or a resistor


Connected to an AC
source

The capacitor
will charge
and discharge

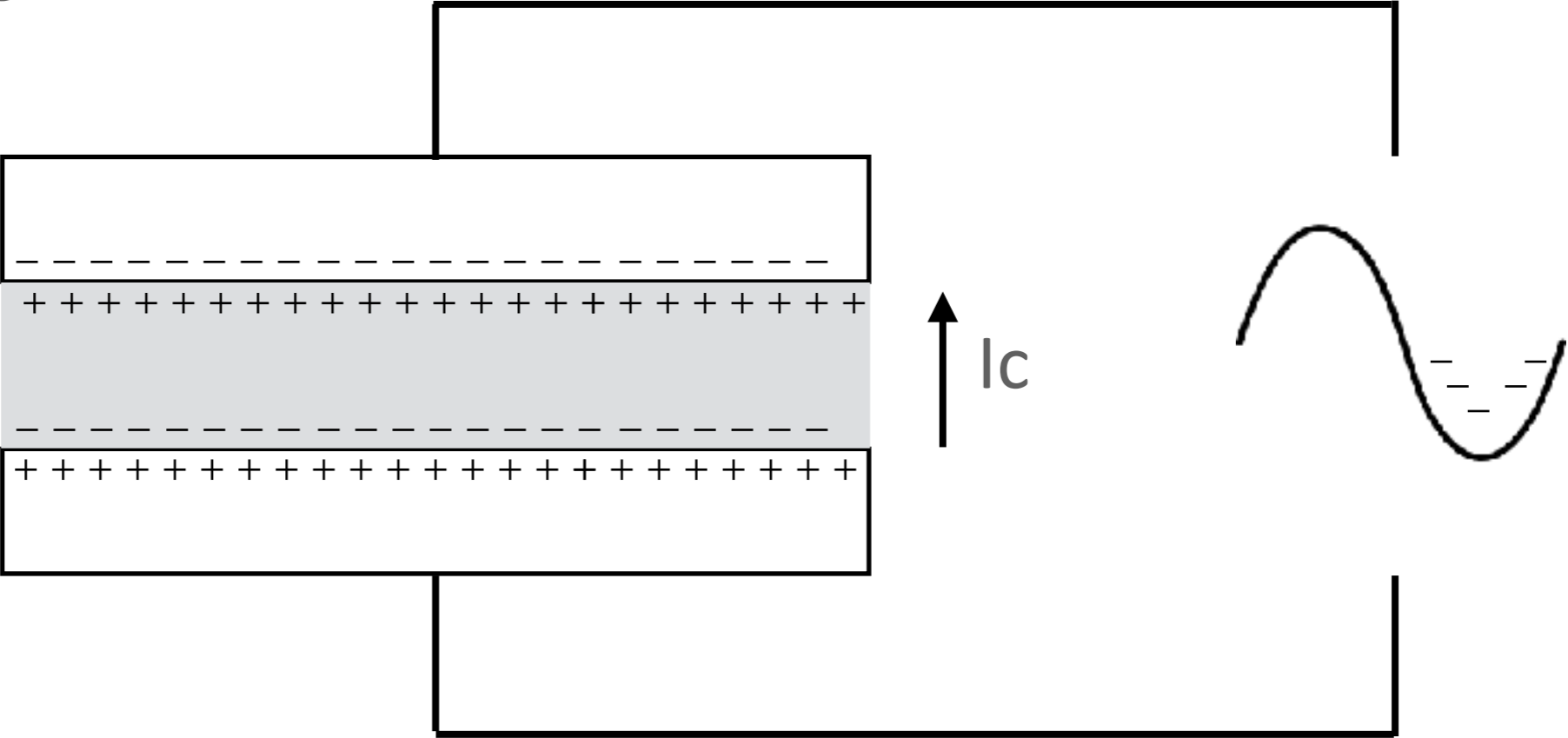


For AC voltage, the Capacitor is a conductor or a resistor

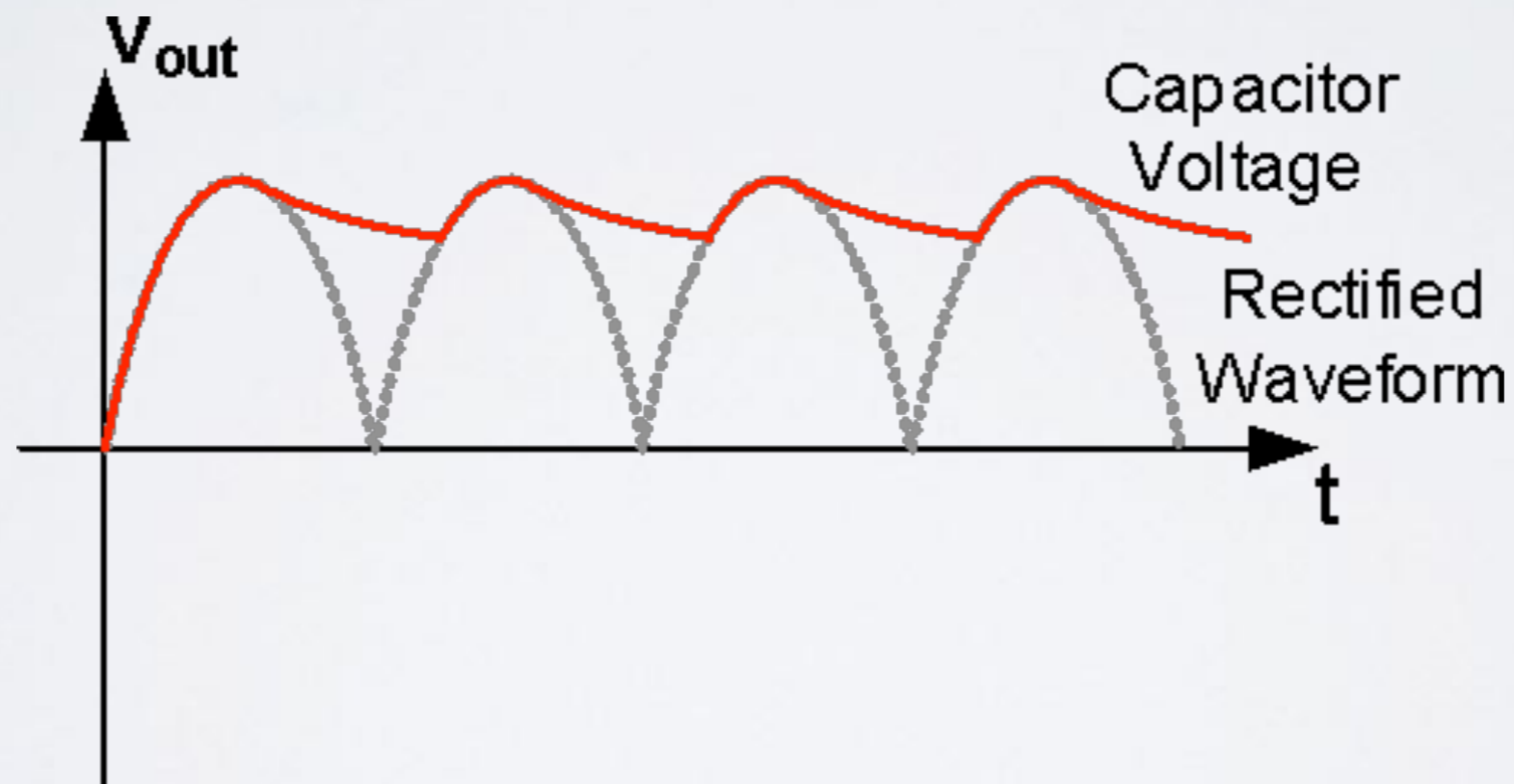So, a **capacitor** is used to smooth the signal ...
The result is a dc-voltage with a “ripple”



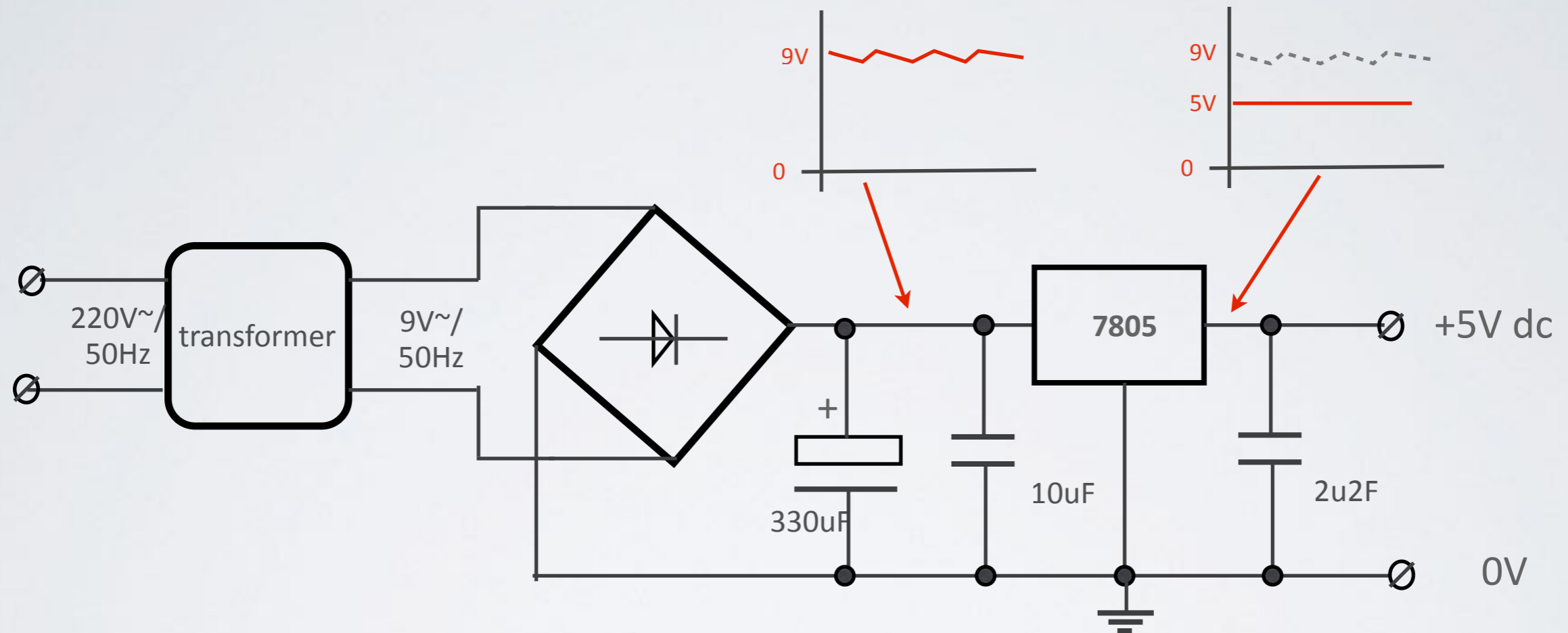To create a **nice and steady DC voltage** (without ripple), we make use of **voltage regulators**.



Voltage regulators exist in all kind of values ...7805, 7806, 7809, 7812, ...7824 ...

Electronics software tools

Circuit simulation examples:

Yenka (www.yenka.com)

<http://www.falstad.com/circuit/>

<http://dcaclab.com/>

iCircuit (mac application)

Partsim (<https://www.partsim.com/simulator#>)

Electronics tools:

Fritzing (from breadboard to circuit/pcb)

Eagle (circuit drawing and pcb design)

Electronics toolbox (mobile app)